












Labeling Electrical Circuits

Label the circuit below.

 battery	 closed switch	 open switch	 cell	 voltmeter
 buzzer	 lamp	 lamp	 motor	 wire

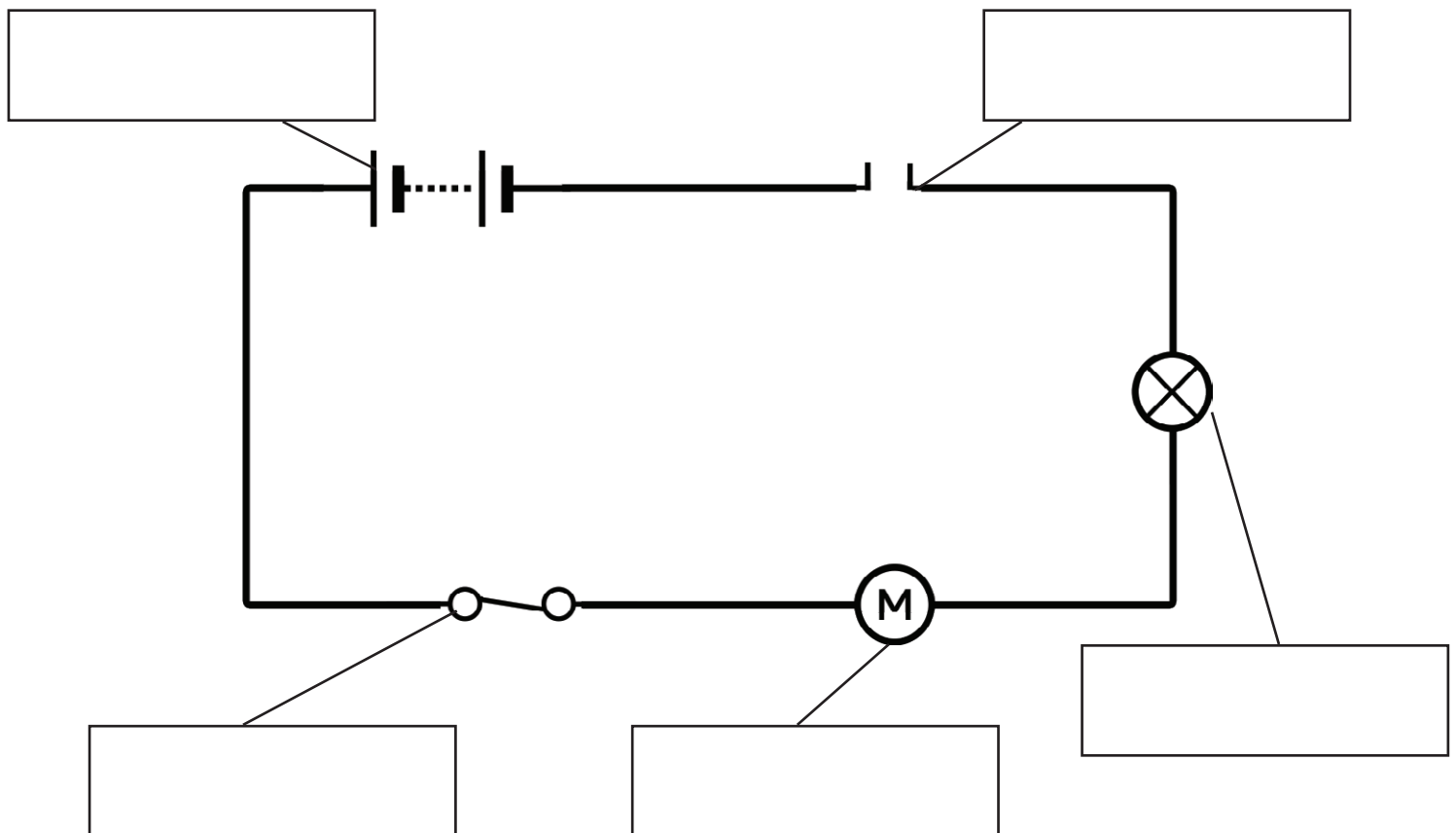

Labeling Electrical Circuits Answer Key

Label the circuit below.

